



Please write clearly in block capitals.

Centre number

--	--	--	--	--

Candidate number

--	--	--	--

Surname _____

Forename(s) _____

Candidate signature _____

I declare this is my own work.

A-level PHYSICS

Paper 3
Section B Electronics

Friday 5 June 2020 Afternoon

Time allowed: The total time for both sections of this paper is 2 hours. You are advised to spend approximately 50 minutes on this section.

- Materials**
For this paper you must have:
- a pencil and a ruler
 - a scientific calculator
 - a Data and Formulae Booklet.

- Instructions**
- Use black ink or black ball-point pen.
 - Fill in the boxes at the top of this page.
 - Answer **all** questions.
 - You must answer the questions in the spaces provided. Do not write outside the box around each page or on blank pages.
 - If you need extra space for your answer(s), use the lined pages at the end of this book. Write the question number against your answer(s).
 - Do all rough work in this book. Cross through any work you do not want to be marked.
 - Show all your working.

For Examiner's Use	
Question	Mark
1	
2	
3	
4	
5	
TOTAL	

- Information**
- The marks for questions are shown in brackets.
 - The maximum mark for this paper is 35.
 - You are expected to use a scientific calculator where appropriate.
 - A Data and Formulae Booklet is provided as a loose insert.



There are no questions printed on this page

*Do not write
outside the
box*

**DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED**




Section B

Answer **all** questions in this section.

0 1

Figure 1 shows part of a circuit that includes a 4-bit binary counter. The main inputs and outputs of the counter are shown.
The counter generates a sequence of binary codes representing the decimal numbers 0 to 7
Output Q_0 is the least significant bit of the binary codes.

Figure 1

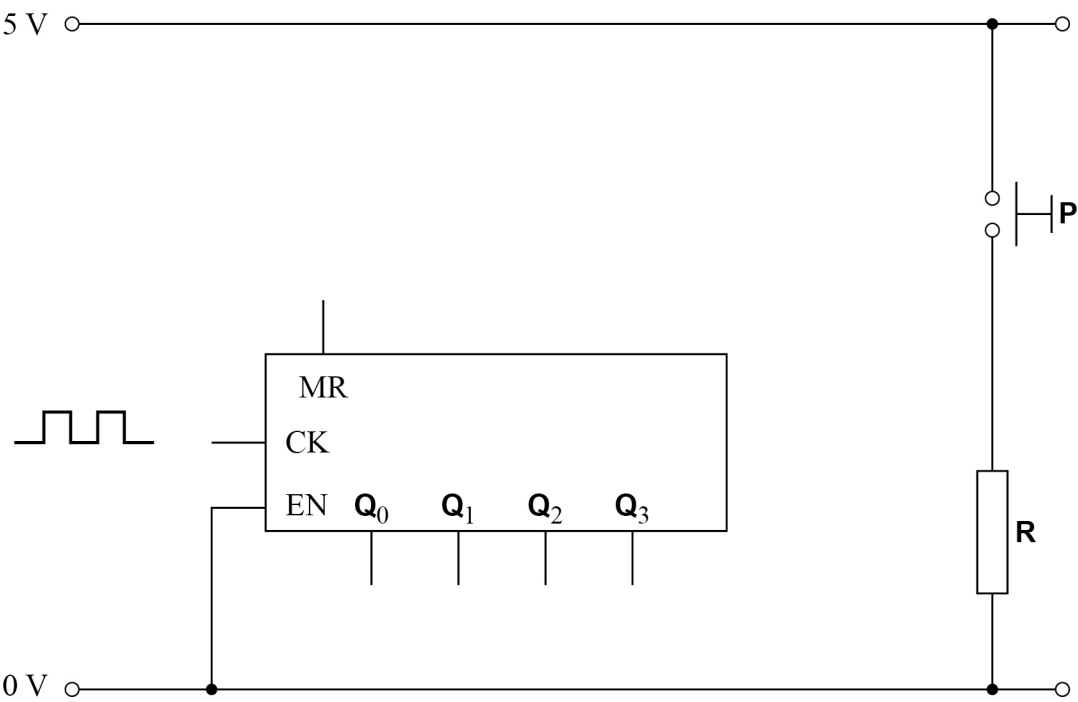

The counter resets when the master reset pin MR receives a logic 1
The circuit requires the counter to reset when either one of two conditions is met.

- Condition 1** Manual reset using the switch **P** to reset the counter to 0
- Condition 2** Automatic reset when an appropriate binary code is produced at the counter outputs. This will cause the counter to continually cycle through the decimal numbers 0 to 7

0 1 . 1

Complete **Figure 1** to show how both reset conditions can be met.
Do **not** show the power line connections to the integrated circuit.

[3 marks]

Question 1 continues on the next page

Turn over ►




0 1 . 2 A logic system is designed to identify prime numbers.

The binary codes from the counter are now applied to the inputs **ABC** of the logic system shown in **Figure 2**.

Input **A** takes the least significant bit of the binary code from the counter.

Output **W** becomes logic state 1 when a prime number 2, 3, 5 or 7 is detected.
Otherwise output **W** is at logic 0

Figure 2

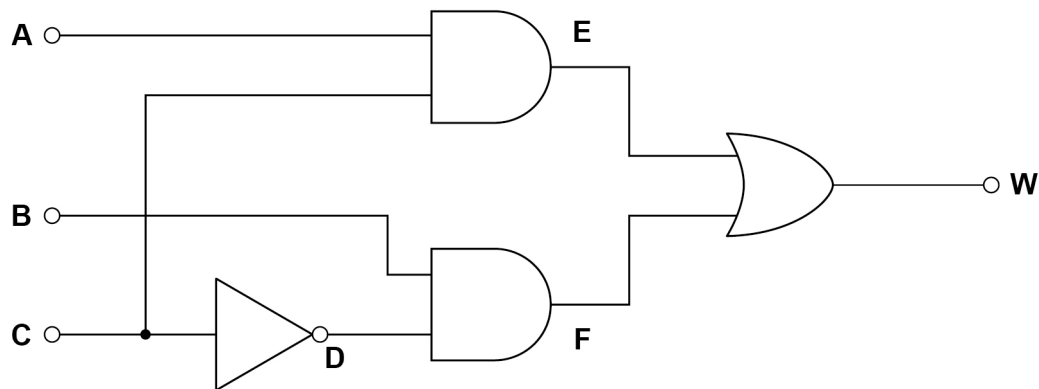

Write the Boolean algebra expression for output **W** in terms of the inputs **A**, **B** and **C**.
The expression must contain only the four logic gate operations shown in **Figure 2**.

[2 marks]

W = _____



01.3

Complete **Table 1**, the truth table for the logic system in **Figure 2**.

[1 mark]

Table 1

Decimal number	C	B	A	D	E	F	W
0	0	0	0	1	0		0
1	0	0	1	1	0		0
2	0	1	0	1	0		1
3	0	1	1	1	0		1
4	1	0	0	0	0		0
5	1	0	1	0	1		1
6	1	1	0	0	0		0
7	1	1	1	0	1		1

01.4

The logic system in Question **01.2** is replaced with one that gives an output **S** using the same binary input codes **CBA**.

The Boolean algebra equation for output **S** is

$$S = \overline{A} \cdot (B + C)$$

Deduce which decimal numbers 0 to 7 will cause **S** to become logic 1

[1 mark]

Question 1 continues on the next page

Turn over ►



01.5

Complete **Figure 3** by drawing the logic system for **S**.

You must use only the logic gate operations given in $S = \overline{A} \cdot (B + C)$

[2 marks]

Figure 3

A ○ —

B ○ —

C ○ —

— ○ S

9



Turn over for the next question

Do not write
outside the
box

DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED

Turn over ►




0	2
---	---

Figure 4 shows the filter circuit that forms the first stage in an amplitude modulated (AM) radio receiver.

The circuit contains a 3.3 mH inductor and a variable capacitor.

Figure 4

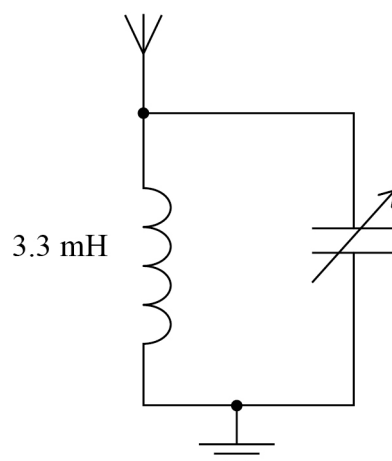

0	2
---	---

1

The circuit is tuned to receive a radio station transmitting at a frequency of 1053 kHz.

Calculate the value of the capacitance needed to receive this station.

[1 mark]

capacitance = _____ pF



0 2 . 2

The circuit is retuned to receive a different radio station by setting the variable capacitor to a value of 9.3 pF.

Table 2 shows the capacitance range of four variable capacitors **W**, **X**, **Y** and **Z**.

Comment on the suitability of these capacitors for this application and state your preference.

[2 marks]

Table 2

Capacitor	Range / pF
W	2–9
X	3–10
Y	4.5–20
Z	10–50

Question 2 continues on the next page

Turn over ►



Do not write
outside the
box


0

2

3

Figure 5 shows part of the frequency response curve for a different filter circuit.

Figure 5

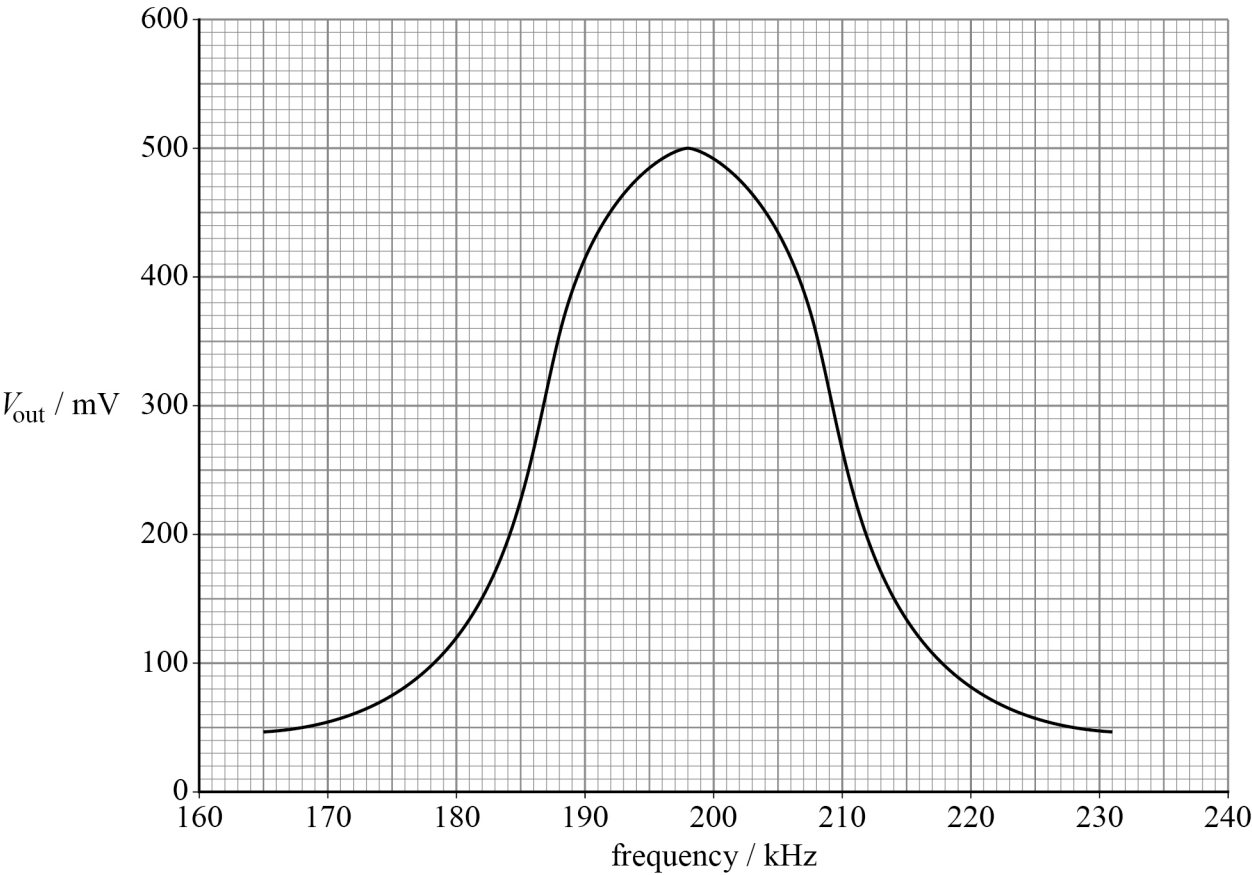

Determine the bandwidth of the filter circuit.

[2 marks]

bandwidth = _____ kHz



Do not write
outside the
box

0 2 . 4

Calculate the Q factor of the filter circuit in Question 02.3.

[1 mark]

Q factor = _____

0 2 . 5

The radio station is tuned using a different filter circuit with a very low Q factor.

State and explain **one** effect of this change on the sound heard by a listener.

[1 mark]

7

Turn over for the next question

Turn over ►



03

Pulse code modulation (PCM) is used to encode live music as an uncompressed digital audio file.
Sampling of the analogue signal is carried out at 44.1 kHz.
A 16-bit system is used to encode each of the two channels that make up the stereo signal.

03.1

Explain why the sampling frequency used is suitable for this task.

[2 marks]

03.2

Calculate the number of quantisation levels available on a 16-bit encoding system.

[1 mark]

number of quantisation levels = _____



Do not write
outside the
box

0 3 . 3

A recorded piece of stereo music lasts for 3.5 minutes.

Calculate the size, in megabytes, of the digital file needed to store this recording.

[2 marks]

file size = _____ megabytes

0 3 . 4

The music file is used by a call centre to play as background music while a phone call is on hold. However, the telephone network is designed to use a bandwidth of 0.3 kHz – 3.4 kHz.

Compare the quality of the music heard by the telephone caller with that of the original file heard when played directly from a compact disc.

[2 marks]

7


Turn over ►



0 4

Figure 6 shows a circuit containing a photodiode and an ideal operational amplifier. This circuit is used to monitor the intensity of monochromatic radiation.

Figure 6

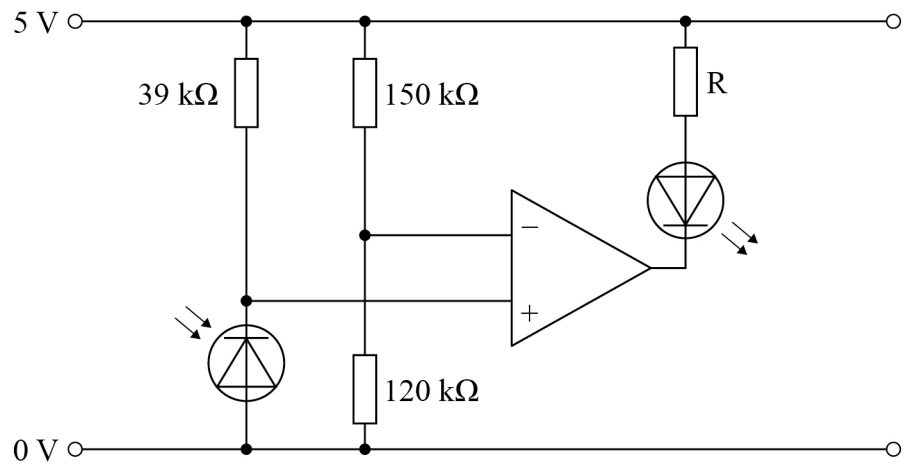

0 4 . 1

What is the configuration of the operational amplifier circuit shown in **Figure 6**? Tick (✓) **one** box.


[1 mark]

- | | |
|-------------------------|--------------------------|
| comparator | ☐ |
| differential amplifier | ☐ |
| inverting amplifier | ☐ |
| non-inverting amplifier | ☐ |



0 4 . 2

Figure 7 shows the variation of photocurrent with intensity for the monochromatic radiation incident on the photodiode.

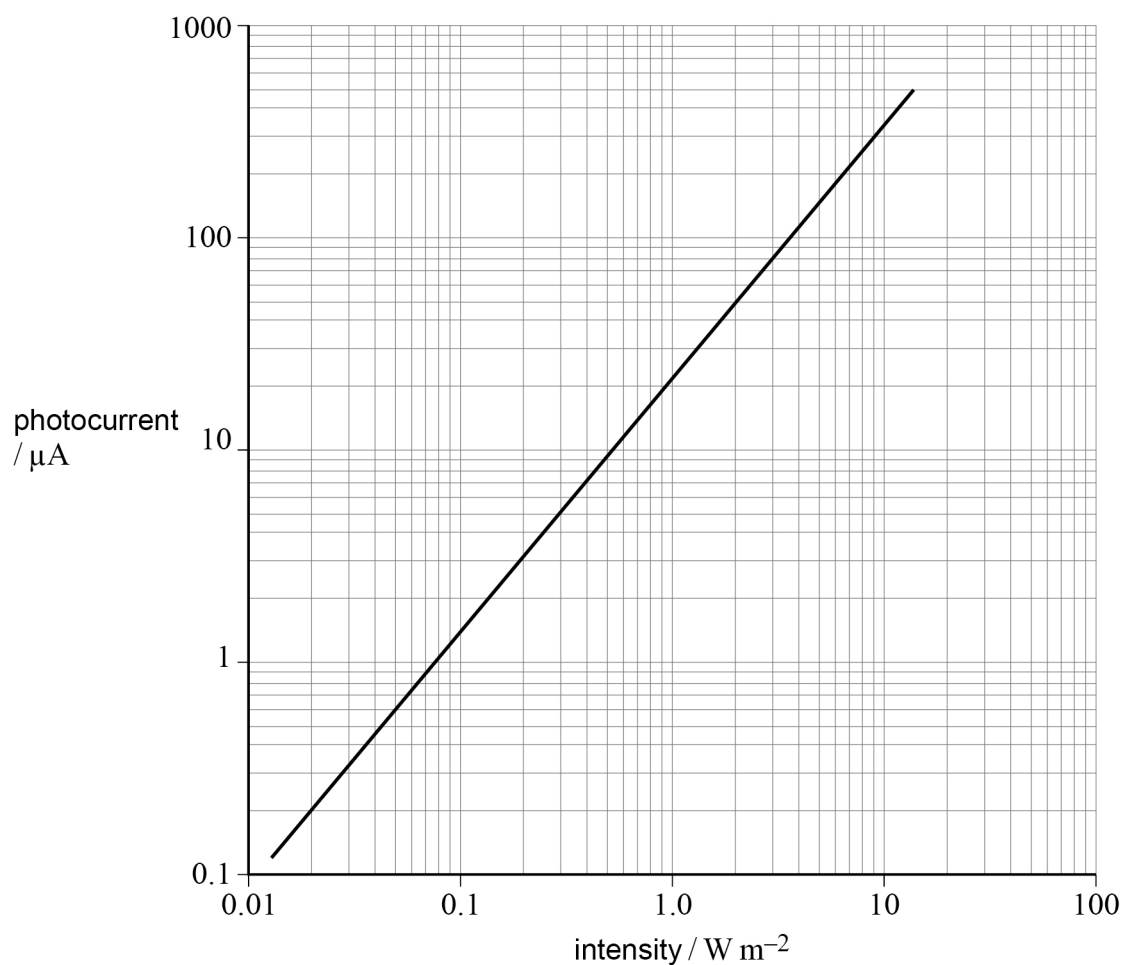Figure 7

Radiation of intensity 3.0 W m^{-2} is incident on the photodiode.

Show that the voltage at the non-inverting terminal (V_+) of the operational amplifier is 1.9 V.

[3 marks]

Question 4 continues on the next page

Turn over ►



Do not write
outside the
box

0 4 . 3

The intensity of radiation incident on the photodiode remains at 3.0 W m^{-2} .

Deduce whether the light-emitting diode (LED) in **Figure 6** is on or off.

[2 marks]

6



There are no questions printed on this page

*Do not write
outside the
box*

**DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED**



[illegible]

[illegible]

[illegible]

[illegible]

There are no questions printed on this page

*Do not write
outside the
box*

**DO NOT WRITE ON THIS PAGE
ANSWER IN THE SPACES PROVIDED**

Copyright information

For confidentiality purposes, all acknowledgements of third-party copyright material are published in a separate booklet. This booklet is published after each live examination series and is available for free download from www.aqa.org.uk.

Permission to reproduce all copyright material has been applied for. In some cases, efforts to contact copyright-holders may have been unsuccessful and AQA will be happy to rectify any omissions of acknowledgements. If you have any queries please contact the Copyright Team.

Copyright © 2020 AQA and its licensors. All rights reserved.



2 4



2 0 6 A 7 4 0 8 / 3 B E

IB/M/Jun20/7408/3BE